

MINISTERUL EDUCAȚIEI NAȚIONALE



UNIVERSITATEA TEHNICĂ
DIN CLUJ-NAPOCA

AUTOMAT DE CUMPARAT BILETE DE TREN

STUDENT:

MOLDOVAN VLAD-MADALIN

COORDONATOR:

OPINCARIU LAURENTIU

Universitate Tehnica din Cluj-Napoca

Facultatea de automatica si calculatoare

Sectia: Calculatoare si tehnologia informatiei

An I , Seria B , Grupa 30217

Continut

1.Specificatie proiect

2.Descriere schema bloc cu componente

3.Lista de componente utilizate si implementare



UNIVERSITATEA TEHNICĂ

DIN CLUJ-NAPOCA

4.Semnificatia notatiilor I/O si a semnalelor interne

5.Justificarea solutiei alese

6.Utilizare si rezultate

7.Posibilitati de dezvoltare ulterioara

1.Specificatie proiect

Enunt:

Să se proiecteze un automat pentru cumpărarea biletelor de tren. Cumpărătorul introduce distanța până la destinație (în zeci de km). Costul biletului și sumele introduse sunt afișate pe afișoare 7 segmente. Moneda utilizată este EURO. Prețul maxim pentru un bilet este de 100 Euro.

Automatul primește suma necesară în hârtii sau monede și eliberează biletele și, eventual, restul.


El dispune de o casă de bani care se încarcă la începutul funcționării cu un număr de hârtii și monede (toate posibilitățile între 1 euro și 50 de euro). Lipsa de bilete, introducerea unei sume mai mici decât costul biletului sau imposibilitatea restituirii restului se semnalizează luminos. Se poate renunța în orice moment la operație, cu restituirea sumei introduse, dacă este cazul.

Proiectul va fi realizat de 1 student.

2.Descriere schema bloc cu componente




Cutia neagra:

 

Componente principale:


Memoria Ram

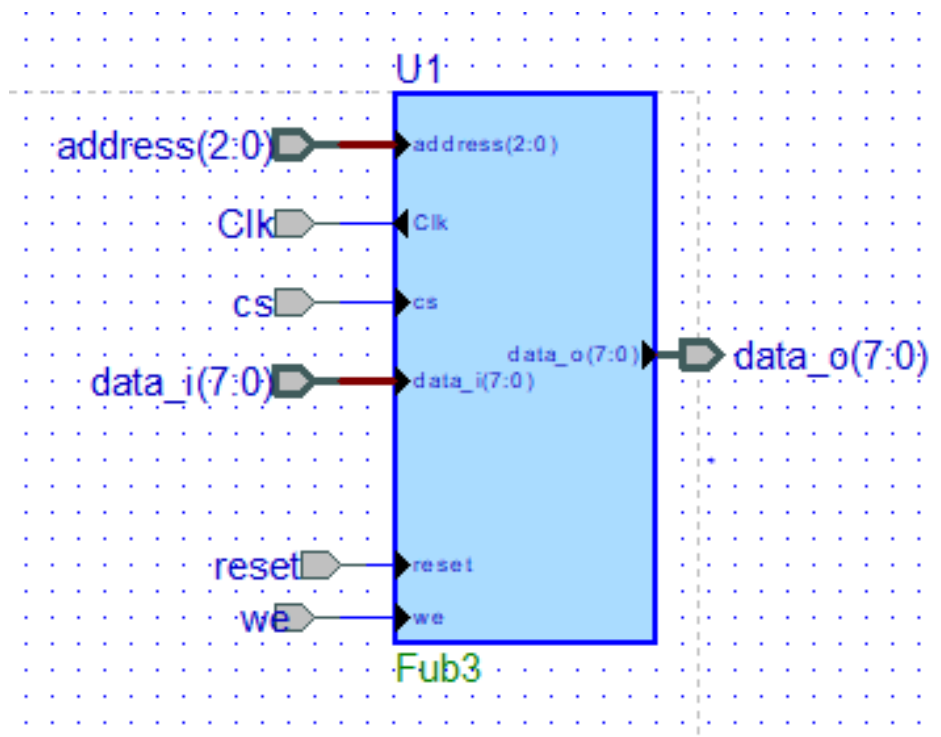Aceasta componenta este folosita pentru a stoca numarul bancnotelor , monedelor si a biletelor de tren.




Suma Totala

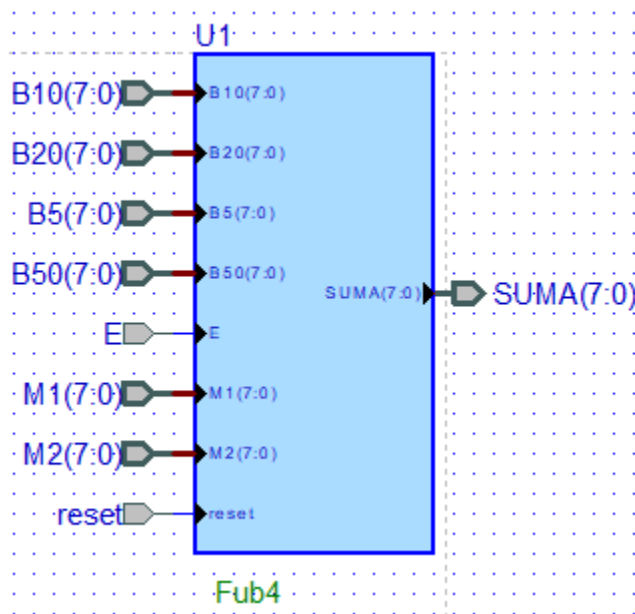Aceasta componenta este folosita pentru a insuma monedele si bancnotele care au fost introduse pentru a obtine suma finala introdusa.



Display

 
Aceasta componenta este utilizata pentru a controla 7-segment display de pe placa FPGA.





Debouncer

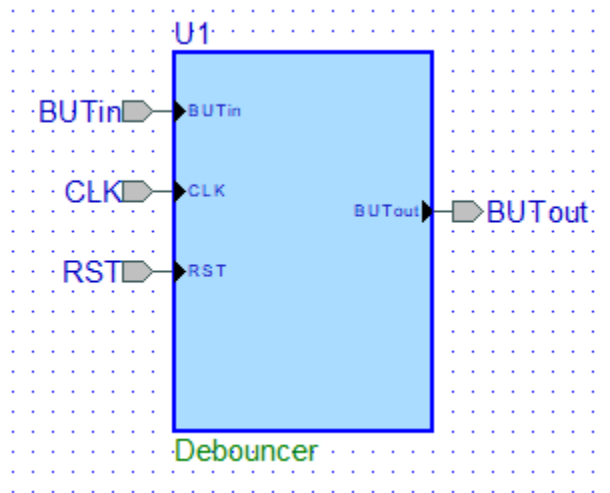Cu ajutorul acestei componente vom obtine semnale stabile pentru utilizarea butoanelor de pe placuta FPGA.



3.Lista de componente utilizate si implementare

Registru:

Aceasta componenta este folosita pentru a fi introdusa distanta de catre cumparator.Contine si un buton de reset pentru cazul in care a fost introdusa gresit distanta initial.

library IEEE;

use IEEE.STD_LOGIC_1164.all;

use IEEE.STD_LOGIC_UNSIGNED.all;

entity reg is

port (data_in: in std_logic_vector (7 downto 0);

reset: in std_logic;

enable: in std_logic;



```
clk: in std_logic;  
data_out: out std_logic_vector (7 downto 0));  
end reg;
```

architecture arh_reg of reg is

begin

process (clk, reset)

begin

if clk='1' and clk'event then

if enable='1' then data_out <= data_in;

end if;

if reset='1' then

data_out<="00000000";

end if;

end if;

end process;

end arh_reg;

Comparator:

Este utilizat pentru a verifica daca suma introdusa este mai mare decat costul , caz afirmativ tranzactia va putea continua.

library IEEE;

use IEEE.STD_LOGIC_1164.all;

use IEEE.STD_LOGIC_UNSIGNED.all;



entity comparator is

```
port(a: in std_logic_vector(7 downto 0);
```

```
b: in std_logic_vector(7 downto 0);
```

```
c: out std_logic_vector(1 downto 0));
```

```
end comparator;
```

architecture arh_comp of comparator is

```
begin
```

```
process(a,b)
```

```
begin
```

```
if (a>b) then c<="01";
```

```
elseif(a<b) then c<="10";
```

```
elseif (a=b) then c<="11";
```

```
end if;
```

```
end process;
```

```
end arh_comp;
```

Scazator:

Este folosit pentru a realiza operatia “-“ pe std_logic_vector.

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.NUMERIC_std.ALL;
```




entity scazator is

port(A: in std_logic_vector (7 downto 0);

B: in std_logic_vector (7 downto 0);

rest: out std_logic_vector (7 downto 0));

end scazator;

architecture arh_scazator of scazator is

begin

process(A,B)

begin

rest <= std_logic_vector(unsigned(A) - unsigned(B));

end process;

end arh_scazator;

Sumator:

Este folosit pentru a realiza operatia “+” pe std_logic_vector.

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_std.ALL;

entity sumator is

port(A: in std_logic_vector (15 downto 0);

B: in std_logic_vector (7 downto 0);

total: out std_logic_vector (15 downto 0));



end sumator;

architecture arh_sumator of sumator is

begin

process(A,B)

begin

total <= std_logic_vector(unsigned(A) + unsigned(B));

end process;

end arh_sumator;

Memoria RAM:

In plus fata de cele mentionate mai sus , “address” va semnifica tipul valoarea monedei/bancnotei astfel: “111” => 50 euro , “110” => 20 euro , “101” => 10 euro , “100” => 5 euro , “011” => 2 euro , “010” => 1 euro , iar pentru combinatia “000” se vor retine numarul de bilete.”Data_i” va reprezenta numarul de bancnote/monede introduse pentru fiecare tip “address”.

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use ieee.std_logic_unsigned.all;

entity memorie is

port (Clk : in std_logic;

address : in std_logic_vector(2 downto 0);

reset : in std_logic;

we : in std_logic;



— UNIVERSITATEA TEHNICĂ —
DIN CLUJ-NAPOCA

```
        cs : in std_logic;
        data_i : in std_logic_vector(7 downto 0);
        data_o : out std_logic_vector(7 downto 0)
    );
end memorie;

architecture arh_memorie of memorie is

    type ram_t is array (7 downto 0) of std_logic_vector(7 downto 0);
    signal ram : ram_t := ("00110111",
        "00110111",
        "00110111",
        "00110111",
        "00110111",
        "00110111",
        "00000000",
        "00110111");

begin

    process(Clk)
    begin
        if Clk = '1' and Clk'EVENT then
            if (CS = '1') then
```



```
if(we='1') then
    ram(conv_integer(address)) <= ram(conv_integer(address)) + data_i;
else
    data_o <= ram(conv_integer(address));
end if;

end if;

if (reset = '1') then
    ram <= ("00110111",
            "00110111",
            "00110111",
            "00110111",
            "00110111",
            "00110111",
            "00000000",
            "00110111");

end if;

end if;

end process;

end arh_memorie;
```

Suma totala:

In plus fata de cele mentionate mai sus , aceasta componenta are un buton de reset care poate fi utilizat pentru a reseta suma introdusa.

library IEEE;



```
use IEEE.std_logic_1164.all;
```

```
use IEEE.NUMERIC_std.all;
```

```
entity Convertor_Suma is
```

```
    port(E: in std_logic;
```

```
         reset: in std_logic;
```

```
         M1: in std_logic_vector(7 downto 0);
```

```
         M2: in std_logic_vector(7 downto 0);
```

```
         B5: in std_logic_vector(7 downto 0);
```

```
         B10: in std_logic_vector(7 downto 0);
```

```
         B20: in std_logic_vector(7 downto 0);
```

```
         B50: in std_logic_vector(7 downto 0);
```

```
         SUMA: out std_logic_vector(7 downto 0));
```

```
end Convertor_Suma;
```

```
architecture Arch_Convertor_Suma of Convertor_Suma is
```

```
begin
```

```
    process(E,M1,M2,B5,B10,B20,B50)
```

```
        variable P0,P1,P2,P3,P4,P5,S: std_logic_vector(15 downto 0);
```

```
    begin
```

```
        if E = '1' then
```

```
            P0 := std_logic_vector(unsigned(M1) * "00000001");
```

```
            P1 := std_logic_vector(unsigned(M2) * "00000010");
```

```
            P2 := std_logic_vector(unsigned(B5) * "00000101");
```



UNIVERSITATEA TEHNICĂ
DIN CLUJ-NAPOCA

```

P3 := std_logic_vector(unsigned(B10) * "00001010");
P4 := std_logic_vector(unsigned(B20) * "00010100");
P5 := std_logic_vector(unsigned(B50) * "00110010");

S := std_logic_vector(unsigned(P0) + unsigned(P1) + unsigned(P2) +
unsigned(P3) + unsigned(P4) + unsigned(P5));

end if;

if reset = '1' then

    P0 := "0000000000000000";
    P1 := "0000000000000000";
    P2 := "0000000000000000";
    P3 := "0000000000000000";
    P4 := "0000000000000000";
    P5 := "0000000000000000";

    S := std_logic_vector(unsigned(P0) + unsigned(P1) + unsigned(P2) +
unsigned(P3) + unsigned(P4) + unsigned(P5));

end if;

SUMA <= S(7 downto 0);

end process;

end Arch_Convertor_Suma;
    
```

Display:

Aceasta componenta opereaza displayul 7-segment a placutei FPGA prin intermediul LED_out si an .

library IEEE;

use IEEE.std_logic_1164.all;



```
use IEEE.NUMERIC_std.all;
```

entity Display is

```
    port(DIN: in std_logic_vector(7 downto 0);  
          CLK: in std_logic;  
          ENABLE: in std_logic;  
          LED_out: out std_logic_vector(6 downto 0);  
          an: out std_logic_vector(3 downto 0)  
    );
```

end Display;

architecture arh_display of Display is

component Binary_BCD is

```
    port(DIN: in std_logic_vector(7 downto 0);  
          Dout: out std_logic_vector(11 downto 0));
```

end component;

component divizor is

```
    generic(N: NATURAL := 4);  
    port(CLK: in std_logic;  
          CE: in std_logic;  
          RST: in std_logic;  
          Q: out std_logic_vector(N-1 downto 0));
```

end component;



```
signal Numar: std_logic_vector(11 downto 0);
signal Countout: std_logic_vector(20 downto 0);
signal SEL: std_logic_vector(1 downto 0);
signal RST: std_logic := not ENABLE;
signal Digit: std_logic_vector(3 downto 0);
begin
    C1: Binary_BCD port map(DIN,Numar);
    C2: divizor generic map(N => 21) port map(CLK,'1',RST,Countout);
    SEL <= Countout(20 downto 19);
    process(SEL,ENABLE)
    begin
        if ENABLE = '1' then
            case SEL is
                when "00" => Digit <= Numar(3 downto 0); an <= "1110";
                when "01" => Digit <= Numar(7 downto 4); an <= "1101";

                when "10" => Digit <= Numar(11 downto 8); an <= "1011";
                when others => an <= "1111";
            end case;
        else
            an <= "1111";
        end if;
    end process;
```




```

process(Digit)
begin
    case Digit is
        when "0000" => LED_out <= "0000001"; -- "0"
        when "0001" => LED_out <= "1001111"; -- "1"
        when "0010" => LED_out <= "0010010"; -- "2"
        when "0011" => LED_out <= "0000110"; -- "3"
        when "0100" => LED_out <= "1001100"; -- "4"
        when "0101" => LED_out <= "0100100"; -- "5"
        when "0110" => LED_out <= "0100000"; -- "6"
        when "0111" => LED_out <= "0001111"; -- "7"
        when "1000" => LED_out <= "0000000"; -- "8"
        when "1001" => LED_out <= "0000100"; -- "9"
        when others => LED_out <= "1111111";
    end case;
end process;
end arh_display;
    
```

Binary to BCD:

Foloseste metoda “shift add 3”, ia valoarea BCD a unui numar de 8 biti i-l face compatibil pentru a fi afisat pe displayul 7-segment. Aceasta metoda este foarte usor de aplicat : folosim o variabila Z definite ca std_logic_vector 19 down to 0 (lungimea este data de numarul de biti a numarului in binar + 12 , numarul de biti folositi pentru a stoca un numar zecimal de 3 cifre in BCD) in care punem intrarea pe pozitia 10 down to 3 si la final numarul nostrum in BCD va fi pe pozitia 19 down to 8.



```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
use IEEE.NUMERIC_std.all;
```

```
entity Binary_BCD is
```

```
    port(DIN: in std_logic_vector(7 downto 0);
```

```
          Dout: out std_logic_vector(11 downto 0));
```

```
end Binary_BCD;
```

```
architecture Arch_Binary_BCD of Binary_BCD is
```

```
begin
```

```
    process(DIN)
```

```
        variable Z:std_logic_vector(19 downto 0);
```

```
    begin
```

```
        for i in 0 to 17 loop
```

```
            Z(i) := '0';
```

```
        end loop;
```

```
        Z(10 downto 3) := DIN;
```

```
        for i in 0 to 4 loop
```

```
            if Z(11 downto 8) > "0100" then
```

```
                Z(11 downto 8) := std_logic_vector(unsigned(Z(11 downto 8)) +  
"0011");
```

```
            end if;
```

```
            if Z(15 downto 12) > "0100" then
```



— UNIVERSITATEA TEHNICĂ —
DIN CLUJ-NAPOCA

```
Z(15 downto 12) := std_logic_vector(unsigned(Z(15 downto 12)) +  
"0011");  
  
    end if;  
  
    Z(19 downto 1) := Z(18 downto 0);  
  
    end loop;  
  
    Dout <= Z(19 downto 8);  
  
    end process;  
  
end Arch_Binary_BCD;
```

Divizor de frecventa:

Este folosit pentru a stabili clock-ul , in special pentru displayul 7-segment.

```
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.NUMERIC_std.all;
```

entity divizor is

```
    generic(N: NATURAL := 4);  
    port(CLK: in std_logic;  
         CE: in std_logic;  
         RST: in std_logic;  
         Q: out std_logic_vector(N-1 downto 0));
```

end divizor;

architecture arh_divizor of divizor is



```
begin
    process(CLK,RST,CE)
        variable count: std_logic_vector(N-1 downto 0) := (others => '1');
        begin
            if CLK='1' and CLK'EVENT then
                if RST='1' then
                    count := (others => '0');
                elsif CE = '1' then
                    count := std_logic_vector(unsigned(count)+"1");
                end if;
            end if;
        end if;

        Q <= count;
    end process;
end arh_divizor;
```

Debouncer:

Este un debouncer simplu folosit cu scopul de a stabili valoarea inputului BUTin si sa o transmita print BUTout.

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.NUMERIC_std.all;
```

entity Debouncer is



```
port(BUTin: in std_logic;
      BUTout: out std_logic;
      RST: in std_logic;
      CLK: in std_logic);
end Debouncer;

architecture arh_debouncer of Debouncer is
  component divizor is
    generic(N: NATURAL := 4);
    port(CLK: in std_logic;
          CE: in std_logic;
          RST: in std_logic;
          Q: out std_logic_vector(N-1 downto 0));
  end component;

  signal delay1,delay2,delay3: std_logic;
  signal Q: std_logic_vector(21 downto 0);
  signal BUT1,BUT2: std_logic;
begin
  L1: divizor generic map (N => 22) port map (CLK,'1',RST,Q);
  process(Q(21),RST,BUTin,BUT2)
  begin
    if RST = '1' or BUTin = '0' or BUT2 = '1' then
      delay1 <= '0';
      delay2 <= '0';
```



UNIVERSITATEA TEHNICĂ
DIN CLUJ-NAPOCA

```
        delay3 <= '0';

    elsif Q(21) = '1' and Q(21)'event then
        delay1 <= BUTin;
        delay2 <= delay1;
        delay3 <= delay2;
    end if;
end process;
BUT1 <= delay1 and delay2 and delay3;
process(CLK)
begin
    if RST = '0' then
        if CLK = '1' and CLK'event then
            BUT2 <= BUT1;
        end if;
    else
        BUT2 <= '0';
    end if;
end process;
BUTout <= BUT2;
end arh_debouncer;
```

MAIN:

```
library IEEE;
```



— UNIVERSITATEA TEHNICĂ —
DIN CLUJ-NAPOCA

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use ieee.std_logic_unsigned.all;
```

entity automat is

```
    port(clk: in std_logic;  
          distanta: in std_logic_vector (7 downto 0);  
          cond: in std_logic_vector(1 downto 0);  
          we,E,Eregistru,reset: in std_logic;  
          address: in std_logic_vector (2 downto 0);  
          a_to_g: out std_logic_vector (6 downto 0);  
          an: out std_logic_vector (3 downto 0);  
          led_err1 : out std_logic;  
          led_err2 : out std_logic;  
          led_err3 : out std_logic;  
          led_bilet : out std_logic;  
          led_rest : out std_logic);
```

end automat;

architecture arh_automat of automat is

component reg is

```
    port (data_in: in std_logic_vector (7 downto 0);  
          reset: in std_logic;  
          enable: in std_logic;
```



```
clk: in std_logic;  
data_out: out std_logic_vector (7 downto 0));  
end component;
```

component comparator is

```
port(a: in std_logic_vector(7 downto 0);  
b: in std_logic_vector(7 downto 0);  
c:out std_logic_vector(1 downto 0));  
end component;
```

component scazator is

```
port(A: in std_logic_vector(7 downto 0);  
B: in std_logic_vector(7 downto 0);  
rest : out std_logic_vector(7 downto 0));  
end component;
```

component sumator is

```
port(A: in std_logic_vector (15 downto 0);  
B: in std_logic_vector (7 downto 0);  
total: out std_logic_vector (15 downto 0));  
end component;
```

component memorie is

```
port (Clk : in std_logic;
```




UNIVERSITATEA TEHNICĂ
DIN CLUJ-NAPOCA

```
        address : in std_logic_vector(2 downto 0);  
        reset : in std_logic;  
we : in std_logic;  
        cs : in std_logic;  
data_i : in std_logic_vector(7 downto 0);  
data_o : out std_logic_vector(7 downto 0)  
);  
end component;
```

component Convertor_Suma is

```
    port(E: in std_logic;  
    reset : in std_logic;  
    M1: in std_logic_vector(7 downto 0);  
    M2: in std_logic_vector(7 downto 0);  
    B5: in std_logic_vector(7 downto 0);  
    B10: in std_logic_vector(7 downto 0);  
    B20: in std_logic_vector(7 downto 0);  
    B50: in std_logic_vector(7 downto 0);  
    SUMA: out std_logic_vector(7 downto 0));  
end component;
```

component Display is

```
    port(DIN: in std_logic_vector(7 downto 0);  
    CLK: in std_logic;
```



— UNIVERSITATEA TEHNICĂ —
DIN CLUJ-NAPOCA

```
ENABLE: in std_logic;  
LED_out: out std_logic_vector(6 downto 0);  
an: out std_logic_vector(3 downto 0));  
end component;
```

component Debouncer is

```
port(BUTin: in std_logic;  
      BUTout: out std_logic;  
      RST: in std_logic;  
      CLK: in std_logic);  
end component;
```

```
signal afisare: std_logic_vector(7 downto 0);
```

```
signal data_o: std_logic_vector (7 downto 0);
```

```
signal ok: std_logic_vector (1 downto 0);
```

```
signal ram : std_logic_vector (7 downto 0);
```

```
signal cost: std_logic_vector (7 downto 0);
```

```
signal rest: std_logic_vector (7 downto 0);
```

```
signal M1: std_logic_vector(7 downto 0) := "00000000";
```

```
signal M2: std_logic_vector(7 downto 0) := "00000000";
```

```
signal B5: std_logic_vector(7 downto 0) := "00000000";
```

```
signal B10: std_logic_vector(7 downto 0) := "00000000";
```



UNIVERSITATEA TEHNICĂ
DIN CLUJ-NAPOCA

```

signal B20: std_logic_vector(7 downto 0) := "00000000";
signal B50: std_logic_vector(7 downto 0) := "00000000";
signal SUMA: std_logic_vector(7 downto 0);
signal total: std_logic_vector(15 downto 0);
signal dreset,RST: std_logic;

begin

    c0: Debouncer port map (reset,dreset,RST,clk);
    c1: reg port map (distanta,dreset,Eregistru,clk,cost);
    c2: memorie port map (clk,address,dreset,we,'1',distanta,data_o);
    c3: Convertor_Suma port map(E,dreset,M1,M2,B5,B10,B20,B50,SUMA);
    c4: comparator port map (SUMA,cost,ok);
    c5: scazator port map (SUMA,cost,rest);
    c6: sumator port map("0001000111010000",SUMA,total);
    c7: display port map(afisare,clk,'1',a_to_g,an);

process(cond)
begin
    case cond is
        when "11" => afisare <= cost;
        when "01" => afisare <= suma;
        when "10" => afisare <= rest;
        when others => afisare <= "00000000";
    end case;
end process;

```



UNIVERSITATEA TEHNICĂ
DIN CLUJ-NAPOCA

```
process(address)
begin
    case address is
        when "111" => B50 <= distanta;
        when "110" => B20 <= distanta;
        when "101" => B10 <= distanta;
        when "100" => B5 <= distanta;
        when "011" => M2 <= distanta;
        when "010" => M1 <= distanta;
        when others => NULL;
    end case;
end process;

process(ok,data_o)
begin
    if(data_o > "00000000") then
        led_err1 <= '0';
    else
        led_err1 <= '1';
    end if;
    if(ok="10") then
        led_err2<='1';
        led_rest<='0';
        led_bilet<='0';
    end if;
end process;
```



UNIVERSITATEA TEHNICĂ

DIN CLUJ-NAPOCA

```
elsif (ok="01") then
    led_err2<='0';
    led_rest<='1';
    if(total - rest > "00000000") then
        led_err3 <='0';
    else
        led_err3 <='1';
    end if;
    led_bilet<='1';
elsif (ok="11") then
    led_err2<='0';
    led_rest<='0';
    if(SUMA > "00000000") then
        led_bilet<='1';
    else
        led_bilet<='0';
    end if;
end if;
end process;
end arh_automat;
```



4.Semnificatia notatiilor

Registru:

data_in: distanta introdusa

reset: buton de reset

enable: enable pentru componenta

clk: semnalul de clock de pe FPGA

data_out: distanta memorata

Comparator:

a: suma introdusa

b: costul biletului

c: rezultatul comparatiei

Memorie ram:

clk: semnalul de clock de pe FPGA

address: tipul bancnotei/monedei

reset: buton de reset

we: write enable

cs: chip select

data_i: numarul de bancnote/monede introduse

data_o: outputul memoriei

Suma totala:



UNIVERSITATEA TEHNICĂ

DIN CLUJ-NAPOCA

E: enable pentru componenta

Reset: buton de reset

M1: numarul de monede de 1 euro introduse

M2: numarul de monede de 2 euro introduse

B10: numarul de bancnote de 10 euro introduse

B20: numarul de bancnote de 20 euro introduse

B50: numarul de bancnote de 50 euro introduse

SUMA: suma totala introdusa.

Scazator:

A: suma introdusa

B: distanta introdusa

rest: rezultatul A-B

Sumator:

A: suma din casa de bani in stare initiala

B: suma introdusa

Total: rezultatul A+B

Display:

DIN: numarul care trebuie afisat

CLK: semnalul de clock de pe FPGA

ENABLE: enable pentru componenta

LED_out: controleaza semnalul catodilor

an: controleaza semnalul anozilor



— UNIVERSITATEA TEHNICĂ —
DIN CLUJ-NAPOCA

Divizor frecventa:

CLK: semnalul de clock de pe FPGA

CE: enable pentru semnalul de clock

RST: buton de reset

Q: output

Binary to bcd:

DIN: numarul pe 8 biti in binar

Dout: numarul corespunzator in BCD pe 12 biti

Debouncer:

BUTin: semnalul initial

BUTout: semnalul stabilizat

RST: buton de reset pentru componenta

CLK: semnalul de clock de pe FPGA

MAIN:

clk: semnalul de clock de pe FPGA

distanta: distanta introdusa / numarul de bancnote de pe fiecare tip

cond: conditia pentru afisor : “11” => distanta introdusa”, “01” => suma introdusa , “10” => restul.

we: write enable (pentru memoria ram)

E: enable pentru component “suma_totala”

Eregistru: enable pentru registru



— UNIVERSITATEA TEHNICĂ —
DIN CLUJ-NAPOCA

reset: buton de reset

address: tipul bancnotei introduse

a_to_g: controleaza semnalul catozilor

an: controleaza semnalul anozilor

led_err1: led pentru lipsa bilete

led_err2: led pentru cazul in care suma introdusa este mai mica decat costul biletului

led_err3: led care semnaleaza imposibilitatea de a da rest

led_bilet: led pentru a semnala eliberarea biletului

led_rest: led pentru a semnala eliberarea restului


5. Justificarea solutiei alese

Proiectul consta in implementarea unui automat , iar varianta pe care am ales sa o implementez se bazeaza pe controlul din switchuri. O data ce am ales modul in care vreau sa implementez automatul , am incercat sa-l construiesc cat mai simplu si fara a ma complica prea mult. Aproape toate datele de intrare se afla pe switchuri (distanța, tipul bancnotei/monedei , numărul de bancnote/monede, controlul pentru afișor) pentru a face automatul cat mai usor de folosit pentru utilizator.

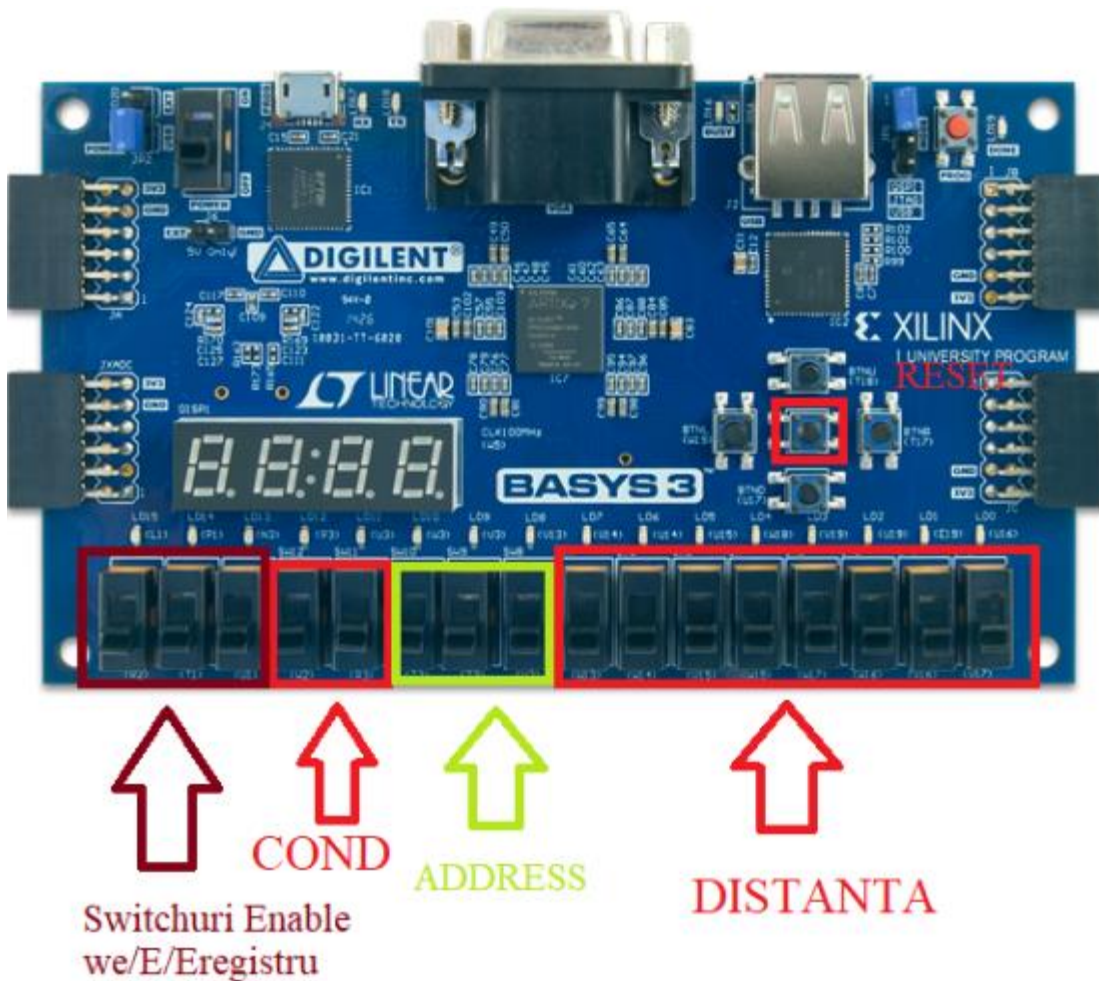6. Utilizare si rezultate



— UNIVERSITATEA TEHNICĂ —
DIN CLUJ-NAPOCA



Folosind maparea din imaginea de mai sus utilizarea automatului va fi mai clara. Prima data se va introduce distanta astfel: se va activa “Eregistru” dupa care se va introduce distanta prin switchurile “distanta” dupa care se va dezactiva “Eregistru”. Al doilea pas consta in introducerea bancnotelor sau monedelor prin activarea “E”, “we” si introducerea combinatiei corespunzatoare pe switchurile “address” (pentru valoare bancnotei / monedei pe care vrem sa o introducem), iar pe switchurile “distanta” vom introduce numarul de bancnote / monede pe care dorim sa le introducem. Pentru a folosi afisorul 7 segment vom introduce pe switchurile “cond” combinatia corespunzatoare pentru ce dorim sa afisam (11=>costul biletului, 01=>suma



— UNIVERSITATEA TEHNICĂ —
DIN CLUJ-NAPOCA

introdusa, $10 \Rightarrow$ restul). În cazul în care s-a introdus ceva greșit, se poate folosi butonul de reset pentru a relua operațiile.

7. Posibilitati de dezvoltare ulterioara

Una dintre îmbunătățirile care ar face acest automat mai funcțional este posibilitatea de a lucra cu numere reale, nu doar întregi. Aceasta îmbunătățire ar face automatul mult mai practic în zilele noastre.